

①

Question 1

	x_4	x_3	x_2	x_1	f
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

2


$x_3 x_4$ $x_1 x_2$	00	01	11	10
00				
01			1	
11		1	1	1
10			1	

$$f = x_1 x_2 x_3 + x_2 x_3 x_4 + x_1 x_4 x_3 + x_1 x_2 x_4$$

$$f = x_1 x_2 (x_3 + x_4) + x_3 x_4 (x_1 + x_2)$$

$$f = \bar{f} = \overline{x_1 x_2 x_3 + x_2 x_3 x_4 + x_1 x_3 x_4 + x_1 x_2 x_4}$$
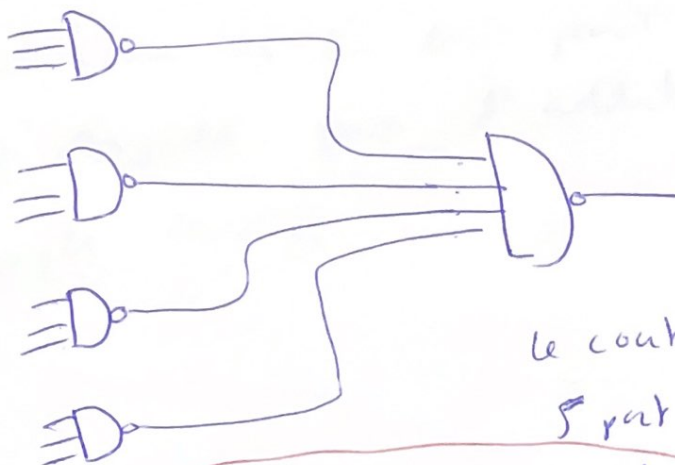
$$f = \overline{x_1 x_2 x_3} \cdot \overline{x_2 x_3 x_4} \cdot \overline{x_1 x_3 x_4} \cdot \overline{x_1 x_2 x_4}$$




le cout est:

5 port NAND + 16

le cout total = 21

Question 2

Part a)

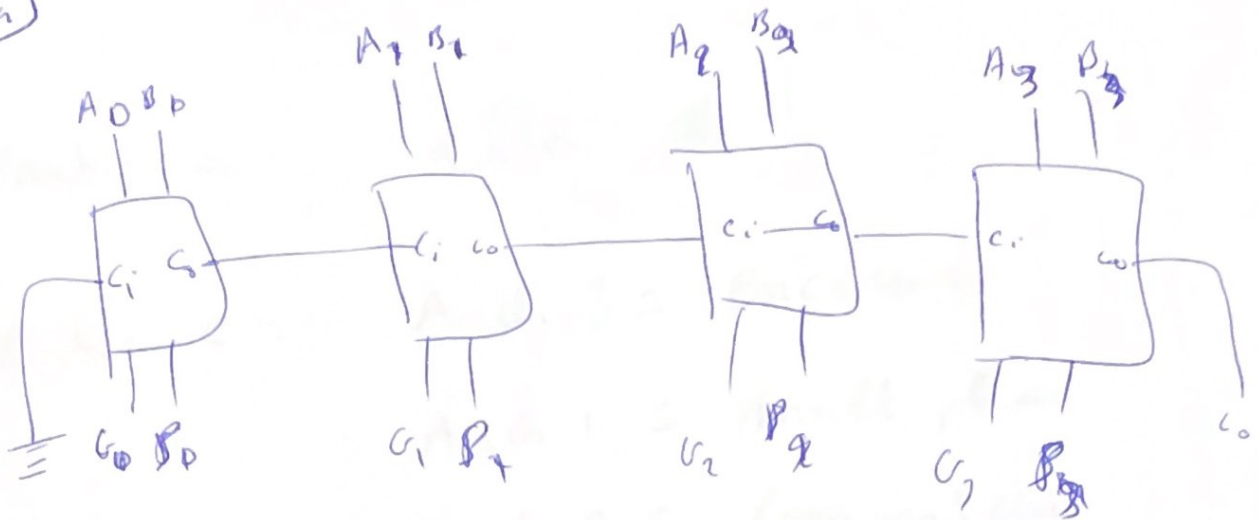

$$C_i = C_{in}$$

$$C_o = C_{out}$$

Part b)

~~La structure plus rapide que l'additionneur~~

~~à 4 bits~~

L'addition comme en part a est plus rapide que l'additionneur ripple carry.

Question III

Part a: alter # 1

Part c: Arch 3 = Encoder

Arch 1 = multiplexer

Arch 2 = Comparator.

~~total~~
entry example is

port (a, b, c : In STD_logic;
 q_a : out STD_logic);

end example.


Question 4

A =

B =

C =

D =

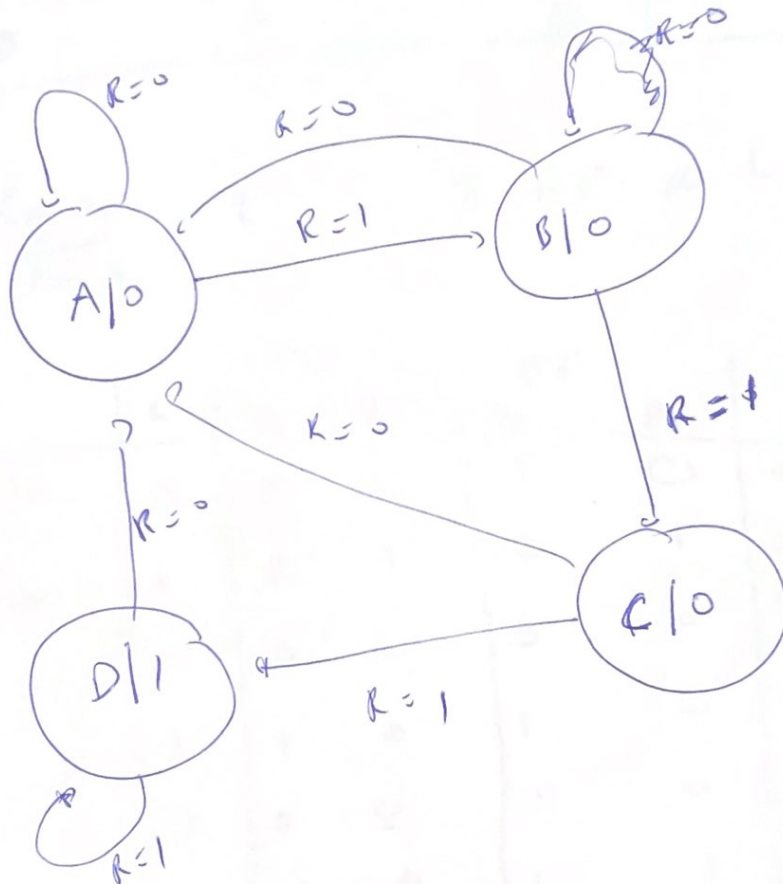

B.S

P.S

output

	P.S		Z
	R=0	R=1	
A	A	B	0
B	A	C	0
C	A	D	0
D	A	D	1

$$m = \frac{\log 4}{\log 2} = 2$$

2 F.F. de Lyre D

P.S	R	P.S		FF		Z
		Y ₂	Y ₁	P _R	P _F	
Y ₂ S ₁	0	0	0	0	0	0
0 0	0	0	0	0	1	0
0 0	1	0	1	0	0	0
0 1	0	0	0	0	0	0
0 1	1	1	0	1	0	0
1 0	0	0	0	1	0	0
1 0	1	1	1	1	1	0
1 1	0	0	0	0	0	1
1 1	1	1	1	1	1	1

P_2

$y_2 y_1$ R	00	01	11	10
0			1	
1		1		1

~~y_2~~

$$D_2 = y_2 y_1 \bar{R} + R(\bar{y}_2 y_1 + y_2 \bar{y}_1)$$

$$D_2 = y_2 y_1 \bar{R} + (y_2 \oplus y_1) R$$

P_1

$y_2 y_1$ R	00	01	11	10
0				1
1	1		1	

$$P_1 = \bar{R}(y_2 \bar{y}_1) + R(\bar{y}_2 \bar{y}_1 + y_2 y_1)$$

$$= \bar{R} y_2 \bar{y}_1 + R(y_2 \odot y_1)$$

Z

$y_2 y_1$ R	00	01	11	10
0			1	
1			1	

$$Z = y_2 y_1$$

