

CEG 3155 and CEG3555: Digital Systems II

Final Exam

Note: Closed book exam. No calculators are allowed.

Name: _____

Student Number: _____

Question	Max. Points	Points
1	15	
2	15	
3	10	
4	30	
5A or 5B	20	
6A or 6B	10	
Total	100	100

Question 1 (5 points each, total 15 points)

Short questions

1. A) Which of these operations is legal in VHDL?


```
SIGNAL a: BIT;  
SIGNAL b: BIT_VECTOR(7 DOWNTO 0);  
SIGNAL c: STD_LOGIC;  
SIGNAL d: STD_LOGIC_VECTOR(7 DOWNTO 0);  
SIGNAL e: INTEGER RANGE 0 TO 255;
```

```
a <= b(5);  
b(0) <= a;  
c <= d(5);  
d(0) <= c;  
a <= c;  
b <= d;
```

```
e <= b;  
e <= d;
```

 
- B) For the following code, draw the waveform for sig_s1, res1 and res2

```
library ieee;  
use ieee.std_logic_1164.all;  
entity sig_var is  
port(    d1, d2, d3:    in std_logic;  
       res1, res2:    out std_logic);  
end sig_var;  
architecture behv of sig_var is  
signal sig_s1: std_logic;  
begin  
  
    proc1: process(d1,d2,d3)  
  
        variable var_s1: std_logic;  
  
    begin  
        var_s1 := d1 and d2;  
        res1 <= var_s1 xor d3;  
    end process;  
  
    proc2: process(d1,d2,d3)  
    begin  
        sig_s1 <= d1 and d2;  
        res2 <= sig_s1 xor d3;  
    end process;  
end behv;
```



C)

 - To design mod-10 counter, you need n -bit register. What is n ?
- For the implementation of the counter below, let setup time of the register to be 0.5 ns and the propagation time from clock to output to be 1 ns. The propagation delays of other components are: incrementor 5ns, comparator 3ns and multiplexer (and other combinational components if any) 0.75 ns. Determine the maximum clock rate.



Question 2 (15 marks)

Write behavioral VHDL code that represents a 24-bit up/down-counter with parallel load and asynchronous reset.

Question 3 (10 marks)

Represent the FSM in Figure 1 in form of an ASM chart.

 


Figure 1

Mealy-type FSM for Question 3.

Question 4 (30 marks)

- a) Design a circuit for controlling the lights used to start a race, which works as follows. There are three inputs: *Reset*, *Start* and *Clock*. There are three outputs: *Red*, *Yellow* and *Green*, which turn on the lights. Only one light can be on at any time. The *Reset* signal forces the circuit into a state in which the red light is turned on. When the *Start* signal is activated, the red light stays on for at least one second longer, then the yellow light is turned on. The yellow light stays turned on about one second and then the green light is turned on. The green light stays on for at least three seconds and then the red light is turned on and the circuit returns to its reset state. Assume that you can use 1 MHz clock.

b) Write VHDL code that can be used to synthesize the circuit specified in Question 4a).

Question 5A (20 marks)

Implement in VHDL the equation $(a * b * c * \text{data_in})$ using pipelining techniques we studied in the class. Note that a , b and c are constants here and the variable ' data_in ' changes every clock cycle. The result of the calculation will be available at the port names ' data_out ' also at every clock cycle. One multiplication operation takes less time than the clock period.

For VHDL of 2-input multiplier please use: $z \leq y * x;$

Question 5B (20 marks)

Derive the minimal flow table that specifies the same functional behavior as the flow table in Figure 3.

Present state	Next state				Output z
	$w_2w_1 = 00$	01	10	11	
A	(A)	B	C	—	0
B	D	(B)	—	—	0
C	P	—	(C)	—	0
D	(D)	E	F	—	0
E	G	(E)	—	—	0
F	M	—	(F)	—	0
G	(G)	H	I	—	0
H	J	(H)	—	—	0
I	A	—	(I)	—	1
J	(J)	K	L	—	0
K	A	(K)	—	—	1
L	A	—	(L)	—	1
M	(M)	N	O	—	0
N	A	(N)	—	—	1
O	A	—	(O)	—	1
P	(P)	R	S	—	0
R	T	(R)	—	—	0
S	A	—	(S)	—	1
T	(T)	U	V	—	0
U	A	(U)	—	—	1
V	A	—	(V)	—	1

Figure 3 Flow table for Question 5B

Question 6A (10 marks)

A one-shot pulse generator is a circuit that generates a single fixed-width pulse upon activation of a trigger signal. We assume that the width of the pulse is N clock cycles. The detailed specifications are listed below.

- There are three input signals, N , go and stop, and one output signal, pulse.
- The go signal is the trigger signal that is usually asserted for only one clock cycle. During normal operation, assertion of the go signal activates the pulse signal for five clock cycles.
- If the go signal is asserted again during this interval, it will be ignored.
- If the stop signal is asserted during this interval, the pulse signal will be cut short and return to '0'.

Show ASMD chart for the one-shot pulse generator.

Question 6B (10 marks)

Find a hazard-free minimum-cost implementation of the function

$$f(x_1, \dots, x_4) = \sum m(0, 4, 11, 13, 15) + D(2, 3, 5, 10)$$

Reference Card

REFERENCE CARD

Revision 2.1

()	Grouping	[]	Optional
{}	Repeated		Alternative
bold	As is	CAPS	User Identifier
<i>italic</i>	VHDL-93	e	commutative
b	::= BIT		
bv	::= BIT_VECTOR		
u/l	::= STD_ULOGIC/STD_LOGIC		
uv	::= STD_ULOGIC_VECTOR		
lv	::= STD_LOGIC_VECTOR		
un	::= UNSIGNED		
sg	::= SIGNED		
in	::= INTEGER		
na	::= NATURAL		
sm	::= SMALL_INT		
	(subtype INTEGER range 0 to 1)		

1. IEEE's STD_LOGIC_1164

1.1. LOGIC VALUES

'U'	Uninitialized
'X'/'W'	Strong/Weak unknown
'0'/'L'	Strong/Weak 0
'1'/'H'	Strong/Weak 1
'Z'	High Impedance
'.'	Don't care

1.2. PREDEFINED TYPES

STD_ULOGIC	Base type
Subtypes:	
STD_LOGIC	Resolved STD_ULOGIC
X01	Resolved X, 0 & 1
X01Z	Resolved X, 0, 1 & Z
UX01	Resolved U, X, 0 & 1
UX01Z	Resolved U, X, 0, 1 & Z

STD_ULOGIC_VECTOR(na to downto na)	Array of STD_ULOGIC
STD_LOGIC_VECTOR(na to downto na)	Array of STD_LOGIC

© 1995-1998 Qualis Design Corporation

1.3. OVERLOADED OPERATORS

Description	Left	Operator	Right
bitwise-and	u/l,uv,lv	and, nand	u/l,uv,lv
bitwise-or	u/l,uv,lv	or, nor	u/l,uv,lv
bitwise-xor	u/l,uv,lv	xor, xnor	u/l,uv,lv
bitwise-not		not	u/l,uv,lv

1.4. CONVERSION FUNCTIONS

From	To	Function
u/l	b	TO_BIT(from[, xmap])
uv,lv	bv	TO_BITVECTOR(from[, xmap])
b	u/l	TO_STDULOGIC(from)
bv,uv	lv	TO_STDLOGICVECTOR(from)
bv,lv	uv	TO_STDULOGICVECTOR(from)

2. IEEE's NUMERIC_STD

2.1. PREDEFINED TYPES

UNSIGNED(na to | downto na) Array of STD_LOGIC
SIGNED(na to | downto na) Array of STD_LOGIC

2.2. OVERLOADED OPERATORS

Left	Op	Right	Return
abs		sg	sg
-		sg	sg
un	+,*,/,rem,mod	un	un
sg	+,*,/,rem,mod	sg	sg
un	+,*,/,rem,mod,c	na	un
sg	+,*,/,rem,mod,c	in	sg
un	<,>,<=,>=,/=	un	bool
sg	<,>,<=,>=,/=	sg	bool
un	<,>,<=,>=,/=c	na	bool
sg	<,>,<=,>=,/=c	in	bool

2.3. PREDEFINED FUNCTIONS

SHIFT_LEFT(un, na)	un
SHIFT_RIGHT(un, na)	un
SHIFT_LEFT(sg, na)	sg
SHIFT_RIGHT(sg, na)	sg
ROTATE_LEFT(un, na)	un
ROTATE_RIGHT(un, na)	un
ROTATE_LEFT(sg, na)	sg
ROTATE_RIGHT(sg, na)	sg
RESIZE(sg, na)	sg
RESIZE(un, na)	un
STD_MATCH(u/l, u/l)	bool
STD_MATCH(u/l, u/l)	bool
STD_MATCH(lv, lv)	bool
STD_MATCH(un, un)	bool
STD_MATCH(sg, sg)	bool

© 1995-1998 Qualis Design Corporation

2.4. CONVERSION FUNCTIONS

From	To	Function
un,lv	sg	SIGNED(from)
sg,lv	un	UNSIGNED(from)
un,sg	lv	STD_LOGIC_VECTOR(from)
un,sg	in	TO_INTEGER(from)
na	un	TO_UNSIGNED(from, size)
in	sg	TO_SIGNED(from, size)

3. IEEE's NUMERIC_BIT

3.1. PREDEFINED TYPES

UNSIGNED(na to | downto na) Array of BIT
SIGNED(na to | downto na) Array of BIT

3.2. OVERLOADED OPERATORS

Left	Op	Right	Return
abs		sg	sg
-		sg	sg
un	+,*,/,rem,mod	un	un
sg	+,*,/,rem,mod	sg	sg
un	+,*,/,rem,mod,c	na	un
sg	+,*,/,rem,mod,c	in	sg
un	<,>,<=,>=,/=	un	bool
sg	<,>,<=,>=,/=	sg	bool
un	<,>,<=,>=,/=c	na	bool
sg	<,>,<=,>=,/=c	in	bool

3.3. PREDEFINED FUNCTIONS

SHIFT_LEFT(un, na)	un
SHIFT_RIGHT(un, na)	un
SHIFT_LEFT(sg, na)	sg
SHIFT_RIGHT(sg, na)	sg
ROTATE_LEFT(un, na)	un
ROTATE_RIGHT(un, na)	un
ROTATE_LEFT(sg, na)	sg
ROTATE_RIGHT(sg, na)	sg
RESIZE(sg, na)	sg
RESIZE(un, na)	un

3.4. CONVERSION FUNCTIONS

From	To	Function
un,bv	sg	SIGNED(from)
sg,bv	un	UNSIGNED(from)
un,sg	bv	BIT_VECTOR(from)
un,sg	in	TO_INTEGER(from)
na	un	TO_UNSIGNED(from)
in	sg	TO_SIGNED(from)

© 1995-1998 Qualis Design Corporation. Permission to reproduce and distribute strictly verbatim copies of this document in whole is hereby granted.

See reverse side for additional information.

VHDL Entity/Architecture

Entity:

entity *entity_name* is

port (*signal_names* : *mode signal_type*;
signal_names : *mode signal_type*;
...
signal_names : *mode signal_type*);

end *entity_name*;

Architecture:

architecture *architecture_name* of *entity_name* is

type declarations
signal declarations
constant declarations
function definitions
procedure definitions
component declarations

begin

concurrent_statement;
...
concurrent_statement;

end *architecture_name*;

VHDL Predefined Types:

bit	character	severity_level
bit_vector	integer	string
boolean	real	time

VHDL Operators:

arithmetic:	+, -, *, /
logical:	and, or, xor, nand, nor, xnor, not
relational:	=, /, <, <=, >, >=
shift left/right logical:	sll, srl
shift left/right arithmetic:	sla, sra
rotate left/right logical:	rol, ror
other:	concatenation: & exponentiation: ** remainder: rem division modulo: mod

VHDL Concurrent Signal Assignments:

Simple Signal Assignment:

signal_name <= *expression*;

Conditional Signal Assignment:

signal_name <= *expression* **when** *boolean_expression* **else**
 expression **when** *boolean_expression* **else**
 ...
 expression **when** *boolean_expression* **else**
 expression;

Selected Signal Assignment:

with *expression* **select**
 signal_name <= *signal_value* **when** *choices*,
 signal_value **when** *choices*,
 ...
 signal_value **when** *others*;

Process:

process (*signal_name*, . . . , *signal_name*)
begin
...
end process;

VHDL Component Declaration:

component *component_name*
 port (*signal_names* : *mode* *signal_type*;
 signal_names : *mode* *signal_type*);
end component;

VHDL if Statement:

if *boolean_expression* **then** *sequential_statement*
end if;
if *boolean_expression* **then** *sequential_statement*
elsif *boolean_expression* **then** *sequential_statement*
 ...
elsif *boolean_expression* **then** *sequential_statement*
else *sequential_statement*
end if;

VHDL Process:

process (*signal_name*, . . . , *signal_name*)
 type declarations
 variable declarations
 constant declarations
 function definitions
 procedure definitions
begin
 sequential_statement
 ...
 sequential_statement
end process;

VHDL Array Declarations:

type *type_name* **is array** (*start to end*) **of** *element_type*;
type *type_name* **is array** (*start* **downto** *end*) **of** *element_type*;
type *type_name* **is array** (*range_type*) **of** *element_type*;
type *type_name* **is array** (*range_type* **range** *start to end*) **of**
 element_type;
type *type_name* **is array** (*range_type* **range** *start* **downto** *end*)
 of *element_type*;

VHDL CONSTANT Declaration:

CONSTANT *const_name* : *signal_type* := *expression*;

VHDL Component Instantiation:

label : *component_name* **port map** (*port_signal_name_1* =>
 signal_1, *port_signal_name_2* => *signal_2*, . . . ,
 port_signal_name_n => *signal_n*);

VHDL Case Statement:

case *expression* **is**
 when *choices* => *sequential_statements*
 ...
 when *choices* => *sequential_statements*
end case;
for loop:
for *identifier* **in** *range* **loop**
 sequential_statement
 ...
 sequential_statement
end loop;