

~~Decake C~~

Gbegbe Decake Jacques

Ottawa

300094197

Devoir 2

ITI 1500

Question 2-3

a) $x y z + x' y + x y z'$

$$f(x, y, z) = x y z + x' y + x y z'$$

$$= x y (z + z') + x' y$$

$$= x y + x' y$$

$$\boxed{f(x, y, z) = y}$$

Car $\forall x, z \in \{0, 1\}$
 $\{x + x' = 1\}$

b) $x' y z + x z$

$$\Rightarrow z (x' y + x) \text{ (distributive)}$$

$$= z (\underbrace{x' + x}_1) (y)$$

$$= z (x + y)$$

$$\boxed{b = z x + y z}$$

c)

$$c) (x + y)(x' + y') = x' y' (x' + y') \text{ (De Morgan)}$$

$$= x' y' x + x' y' y' \text{ (de base)} \quad x + x = x$$

$$= x' y' + x' y' \text{ (de base } x + x = x)$$

$$\boxed{(x + y)(x' + y') = x' y'}$$

$$d) x y + x (w z + w z') = x y + x (w (\underbrace{z + z'}_1)) \text{ (Distributive)}$$

$$= x y + x w$$

(distributive)

$$\boxed{x y + x (w z + w z') = x (y + w)}$$

$$e) (y'z' + x'w')(xy' + zw') = (y'z')(xy') + (y'z')(zw') + (x'w')(xy') + (x'w')(zw') \\ = (yy')(z'x) + (z'z)(yw') + (x'x)(wy') + (ww')(xz')$$

$$\boxed{(y'z' + x'w')(xy' + zw') = 0} \quad (\text{de base } x \cdot x' = 0)$$

$$f) (x' + z')(x + y' + z') = \underbrace{x'x}_{0} + x'y' + x'z' + z'x + z'y' + \underbrace{z'z'}_{z'} \\ = x'y' + z'(x + x') + z'y' + z' \quad (\text{de base } x + x' = 1) \\ = y'(x' + z') + z' + z' \quad (\text{associative}) \\ = z' + y'(z' + x') \\ = z' + y'z' + y'x' \quad (\text{Associative}) \\ = (z' + y'z') + (y'x') \quad (\text{Absorption})$$

$$\boxed{(x' + z')(x + y' + z') = z' + x'y'}$$

Question 2-4

$$a) x'z' + xy'z + xz' = z'(x' + x) + xy'z \quad (\text{de base}) \\ = z' + xy'z$$

$$= \underbrace{(z' + z)}_1 (z' + xy) \quad (\text{Associative})$$

$$\boxed{x'z' + xy'z + xz' = z' + xy}$$

$$\begin{aligned}
 b) (x'y' + z)' + z + xy + wz &= (\overline{x'y'})((x+y)' + z)' + z + xy + wz \\
 &= (\overline{x'y'}) (x+y)z' + z + xy + wz \\
 &= z'x + z'y + z + xy + wz \\
 &= (z+z')(z+x+y) + xy + wz \\
 &= z + wz + x + xy + y \\
 &= z(1+w) + x + y(1+x)
 \end{aligned}$$

$$\boxed{(x'y' + z)' + z + xy + wz = z + x + y}$$

$$\begin{aligned}
 c) w'x(z'y'z) + x(w + w'y'z) &= w'x((z'y')(z+z)) + x((w+y'z) + w + w'y'z) \\
 &= w'x(z'y') + x(w + y'z) \\
 &= x(w'z'y' + w + y'z) \text{ (Distributive)} \\
 &= x(w'z' + w'y' + w + y'z) \\
 &= x(w'z' + (w+y')(w+w') + y'z) \text{ (de base)} \\
 &= x(w'z' + w + y' + y'z) \text{ (de base)} \\
 &= x(w + z' + y + y') \text{ (de base)} \\
 &= x(w + z' + 1)
 \end{aligned}$$

$$\boxed{w'x(z'y'z) + x(w + w'y'z) = x}$$

(par absorption)

$$\begin{aligned}
 d) (w'y)(w'y')(w+x+y'z) &= (w'y y') (w+x+y'z) \quad (\text{Associative}) \\
 &= w'(w+x+y'z) \quad \text{de base } yy' = 0 \\
 &= w'w + w'x + w'y'z \\
 &= w'x + w'y'z \quad (\text{Distributive})
 \end{aligned}$$

$$(w'y)(w'y')(w+x+y'z) = w'(x+y'z)$$

$$\begin{aligned}
 e) wx y'z + w'xz + wxyz &= wxz(y'+y) + w'xz \quad (\text{Associative}) \\
 &= wxz + w'xz \\
 &= xz(w+w') \quad \text{de base } w+w' = 1
 \end{aligned}$$

$$wx y'z + w'xz + wxyz = xz$$

Question 2-11

$$a) F = xy + xy' + y'z$$

x	y	z	y'	xy	xy'	y'z	F
0	0	0	1	0	0	0	0
0	0	1	1	0	0	1	1
0	1	0	0	0	0	0	0
0	1	1	0	0	0	0	0
1	0	0	1	0	1	0	1
1	0	1	1	0	1	1	1
1	1	0	0	1	0	0	1
1	1	1	0	1	0	0	1

b) $F = ac + b'c'$


a	b	c	b'	c'	ac	b'c'	F
0	0	0	1	1	0	1	1
0	0	1	1	0	0	0	0
0	1	0	0	1	0	0	0
0	1	1	0	0	0	0	0
1	0	0	1	1	0	1	1
1	0	1	1	0	1	0	1
1	1	0	0	1	0	0	0
1	1	1	0	0	1	0	1

Question 2-6

Dessiner les circuits logiques qui implément les expressions originales et simplifiées de 2-3 et 6.

a) $xyz + x'y + xyz'$



$F = y$

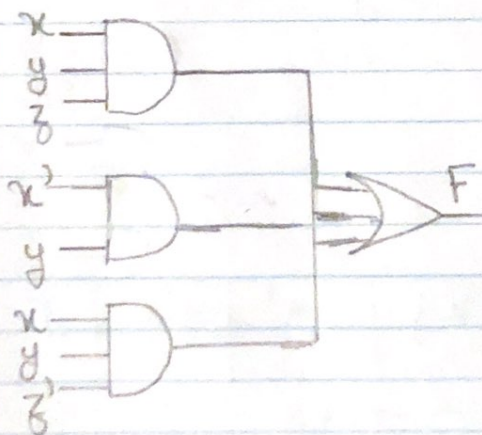

$y = F$



c) $(x+y)'(x'+y')$

$F = x'y'$

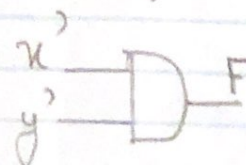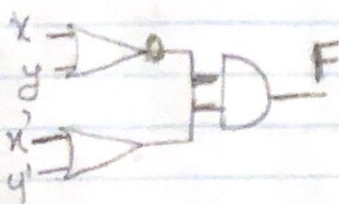


$$f) (x' + z')(x + y' + z')$$

$$F = z' + x'y'$$

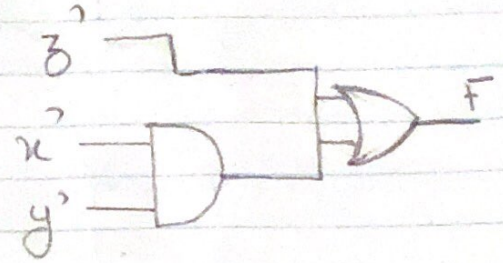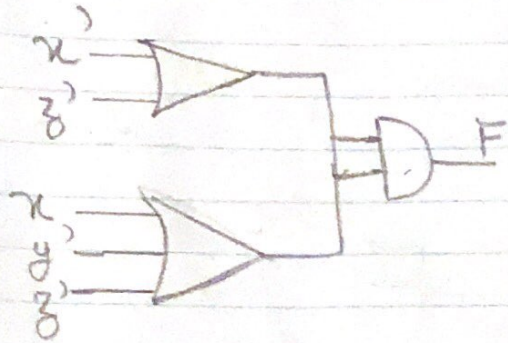

Question 2-7


$$2-4) c) w'x(z' + y'z) + x(w + w'y'z)$$

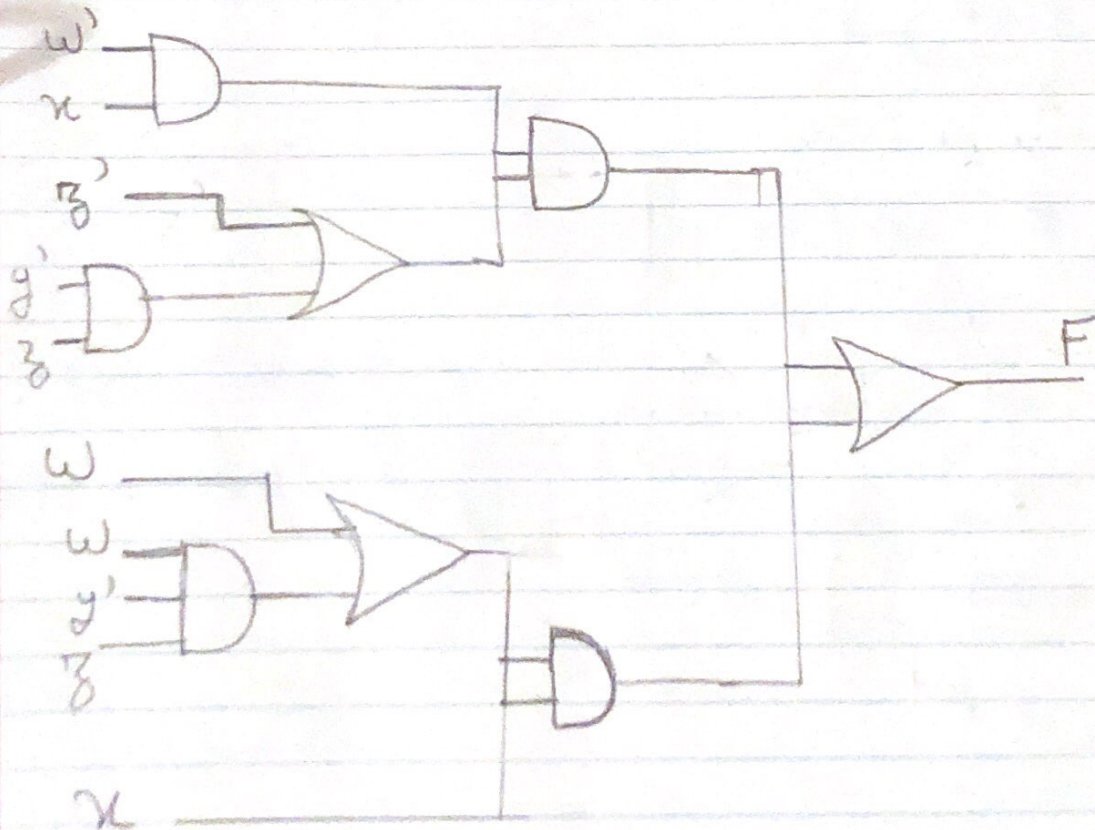


$$F = x$$

$$x \text{ ————— } F$$


2-4) d) $(w' + y)(w' + y')(w + x + y'z)$

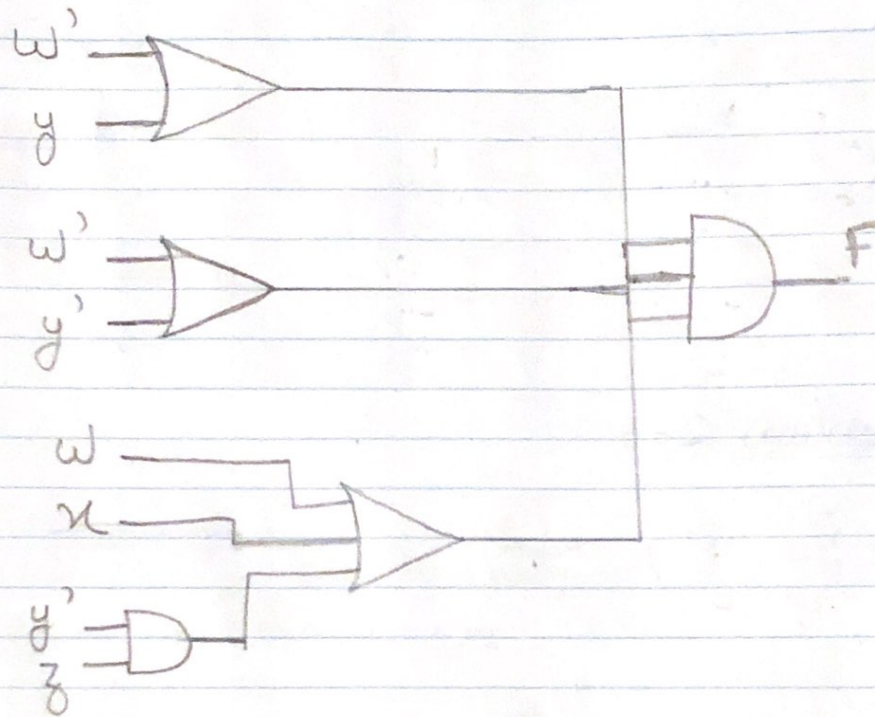

$F = w'(x + y'z)$

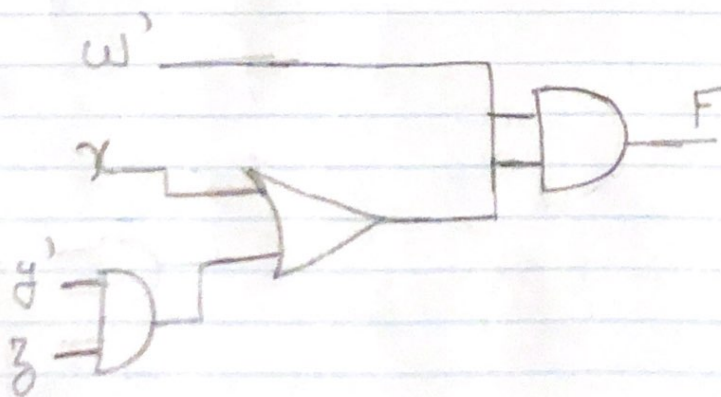

2-4)e) $wxy'z + w'xz + wxyz$

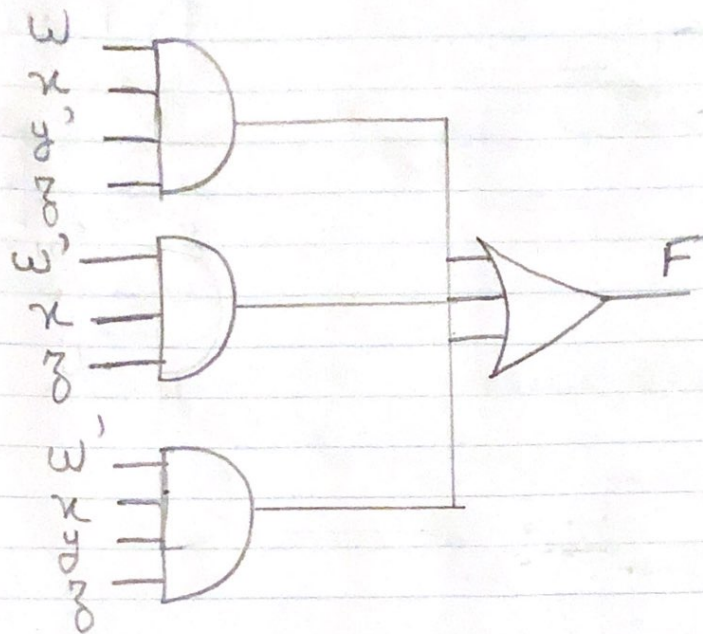


$F = xz$




Questions 2-13


a) $F = (u + x')(y' + z)$

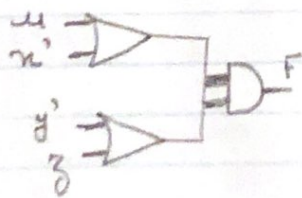


b) $F = (u \oplus y)' + x$

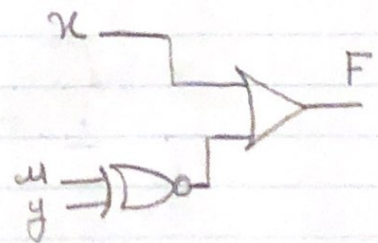


c) $F = (u' + x')(y + z')$

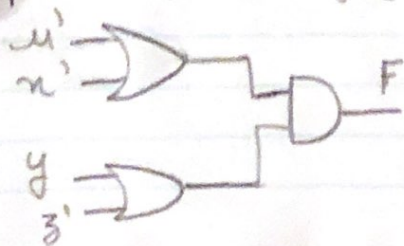

d) $F = u(x \oplus z) + y'$

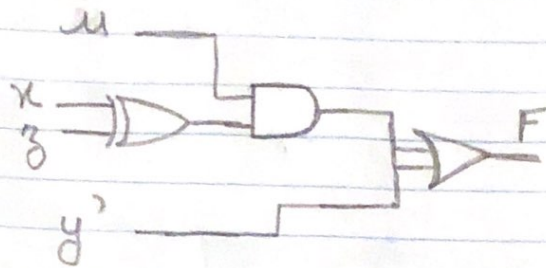


e) $F = u + yz + uxy$

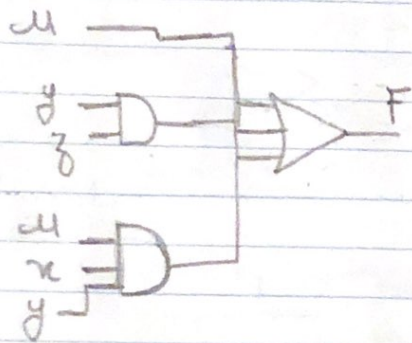


Question 2-14

$F = xy + x'y' + y'z$

a)

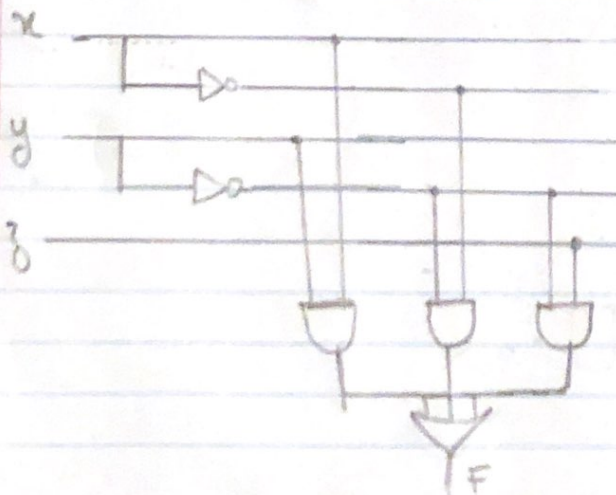


f) $F = u + x + x'(u + y')$

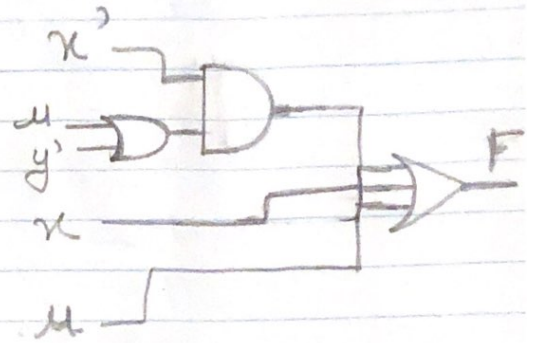


b) en utilisant les lois pour supprimer les ET $\Rightarrow F = (x'y)' + (x+y)' + (y+z)'$

(17) et (9)

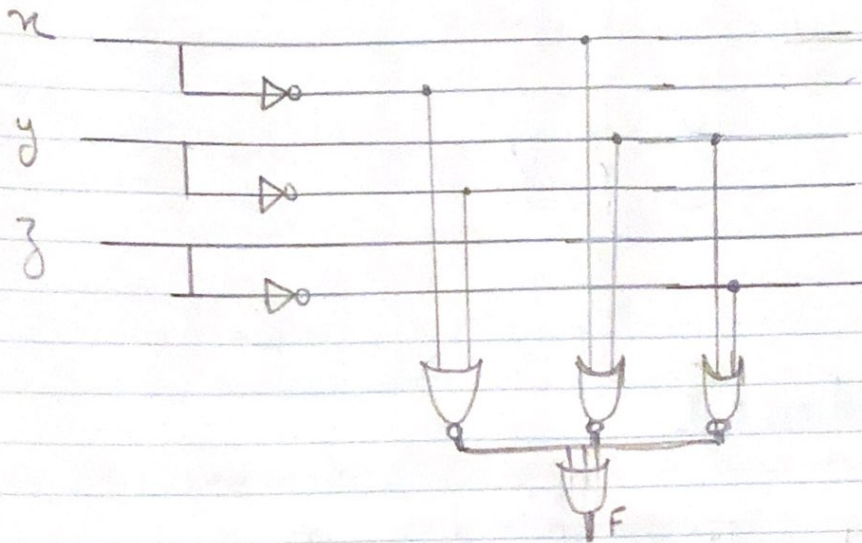


$$F = \begin{cases} xy = (x'y) \\ x'y = (x+y)' \\ y'z = (y+z)' \end{cases}$$

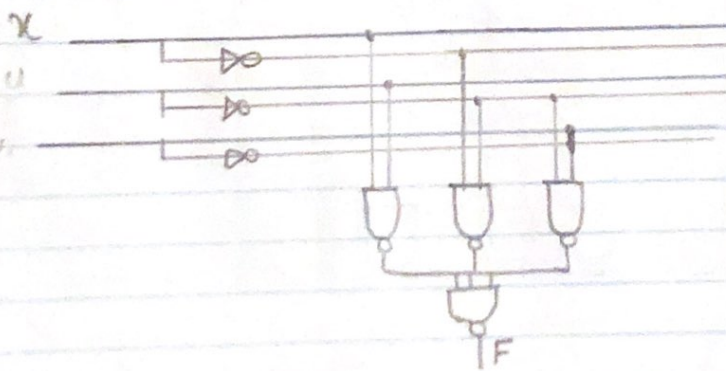c) En utilisant les lois on obtient $\Rightarrow F = ((xy)'(x'y)'(y'z))'$



$$F = \begin{cases} (xy + x'y + y'z)' & (16) \\ ((xy)'(x'y)'(y'z))' & (9) \end{cases}$$

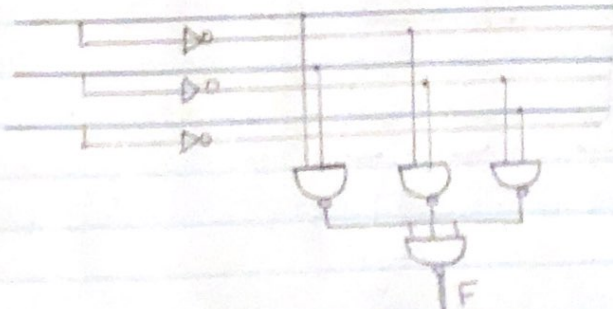
d) En utilisant les lois on obtient $F = [((xy)'(x'y)'(y'z))']'$



$$F = \begin{cases} (xy + x'y + y'z)' & (16) \\ ((xy)'(x'y)'(y'z))' & (9) \end{cases}$$

Milroy

c) En utilisant Non-OU et (Non) $F = \left[((x+y)' + (x+y)' + (y+z)')' \right]'$

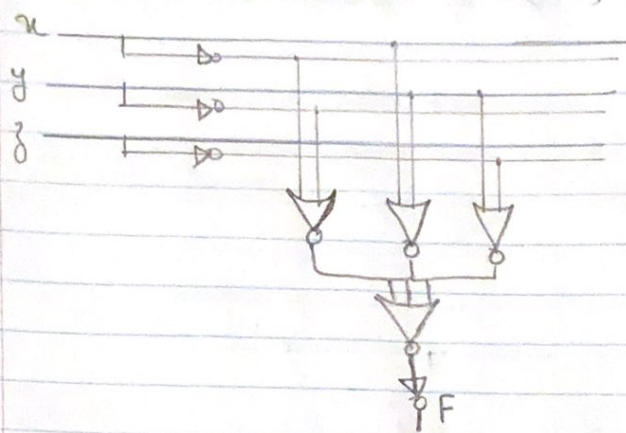


Question 2-18

a) table de vérité de $F = xy'z + x'y'z + w'xy + wx'y + wxy$

w	x	y	z	$xy'z$	$x'y'z$	$w'xy$	$wx'y$	wxy	F
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	1
0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0	0	0
0	1	0	0	1	0	0	0	0	1
0	1	0	1	0	0	0	0	0	0
0	1	1	0	0	0	1	0	0	1
0	1	1	1	0	0	0	1	0	1
1	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0
1	1	0	0	1	0	0	0	0	1
1	1	0	1	0	0	0	0	0	0
1	1	1	0	0	0	1	1	1	1
1	1	1	1	0	0	0	0	1	1

b) Circuit de f.

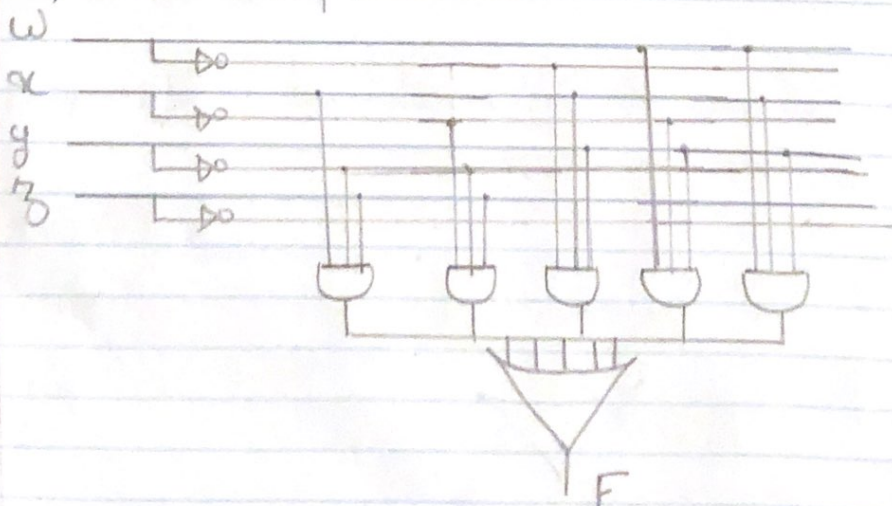

$$c) F = x y' z + x' y' z + w' x y + w x' y + w x y$$

$$= x y (w' + w) + z (x y' + x' y') + w x' y \quad \} \textcircled{3}, \textcircled{14}$$

$$= x y + z y' + w x' y \quad \downarrow \textcircled{14}$$


$$= y (w x' + x) + z y' \quad \downarrow \textcircled{15}$$

$$F = y (x + w) + z y'$$

d) Table de vérité de $F = y (x + w) + z y'$

w	x	y	z	x+w	y(x+w)	z y'	F
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	1
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	1	1
0	1	1	0	1	1	0	1
0	1	1	1	1	1	0	1
1	0	0	0	1	0	0	0
1	0	0	1	1	0	1	1
1	0	1	0	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	1
1	1	1	0	1	1	0	1
1	1	1	1	1	1	0	1

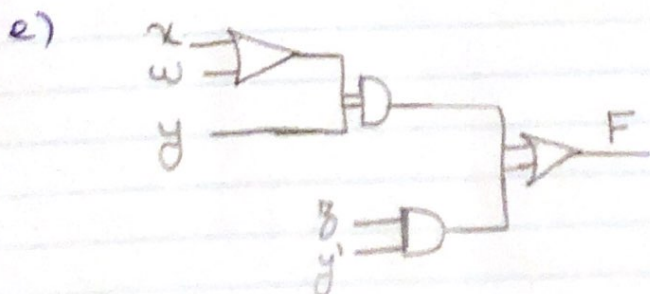La table de vérité en (d) correspond à celle en (a) : Ce sont les mêmes.



* Circuit simplifié à 3 portes "Et" de moins et est plus lisible facilement que le circuit en (b).